

DATA SHEET

For a complete data sheet, please also download:

- The IC04 LOCMOS HE4000B Logic Family Specifications HEF, HEC
- The IC04 LOCMOS HE4000B Logic Package Outlines/Information HEF, HEC

HEF4013B **flip-flops** Dual D-type flip-flop

Product specification
File under Integrated Circuits, IC04



January 1995

Dual D-type flip-flop

HEF4013B
flip-flops

DESCRIPTION

The HEF4013B is a dual D-type flip-flop which features independent set direct (S_D), clear direct (C_D), clock inputs (CP) and outputs (O, $\overline{O}$). Data is accepted when CP is LOW and transferred to the output on the positive-going edge of the clock. The active HIGH asynchronous clear-direct (C_D) and set-direct (S_D) are independent and override the D or CP inputs. The outputs are buffered for best system performance. Schmitt-trigger action in the clock input makes the circuit highly tolerant to slower clock rise and fall times.

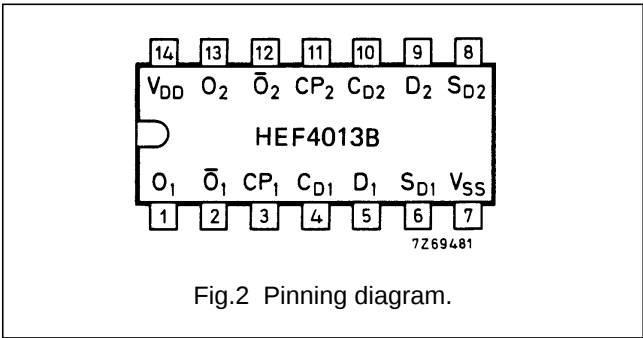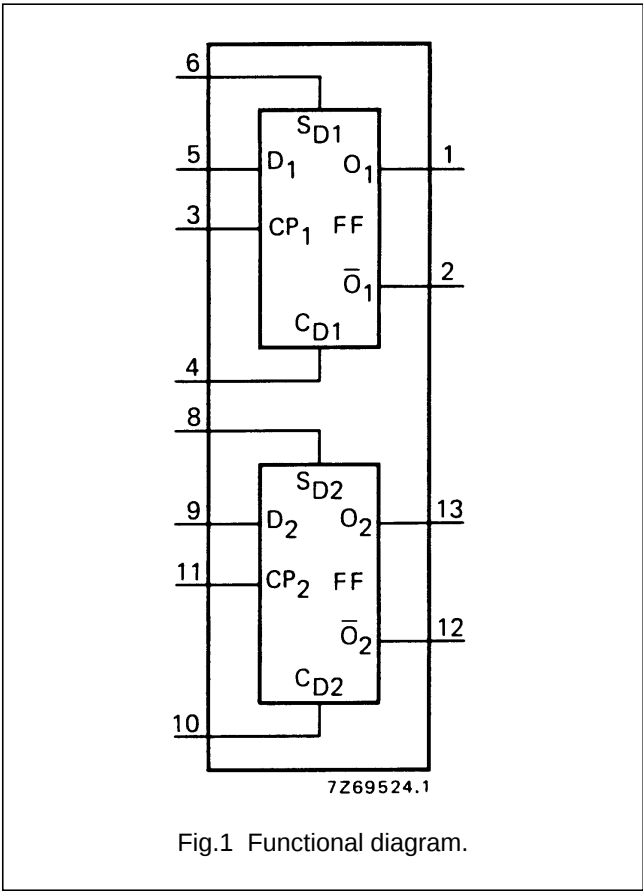

FUNCTION TABLES

INPUTS				OUTPUTS	
S_D	C_D	CP	D	O	$\overline{O}$
H	L	X	X	H	L
L	H	X	X	L	H
H	H	X	X	H	H

INPUTS				OUTPUTS	
S_D	C_D	CP	D	$O_n + 1$	$\overline{O_n} + 1$
L	L		L	L	H
L	L		H	H	L

Notes

- 1. H = HIGH state (the more positive voltage)
L = LOW state (the less positive voltage)
X = state is immaterial
 = positive-going transition
 $O_n + 1$ = state after clock positive transition

PINNING

- D data inputs
- CP clock input (L to H edge-triggered)
- S_D asynchronous set-direct input (active HIGH)
- C_D asynchronous clear-direct input (active HIGH)
- O true output
- $\overline{O}$ complement output

- HEF4013BP(N): 14-lead DIL; plastic (SOT27-1)
- HEF4013BD(F): 14-lead DIL; ceramic (cerdip) (SOT73)
- HEF4013BT(D): 14-lead SO; plastic (SOT108-1)
- (): Package Designator North America

FAMILY DATA, I_{DD} LIMITS category FLIP-FLOPS

See Family Specifications

Dual D-type flip-flop

HEF4013B
flip-flops

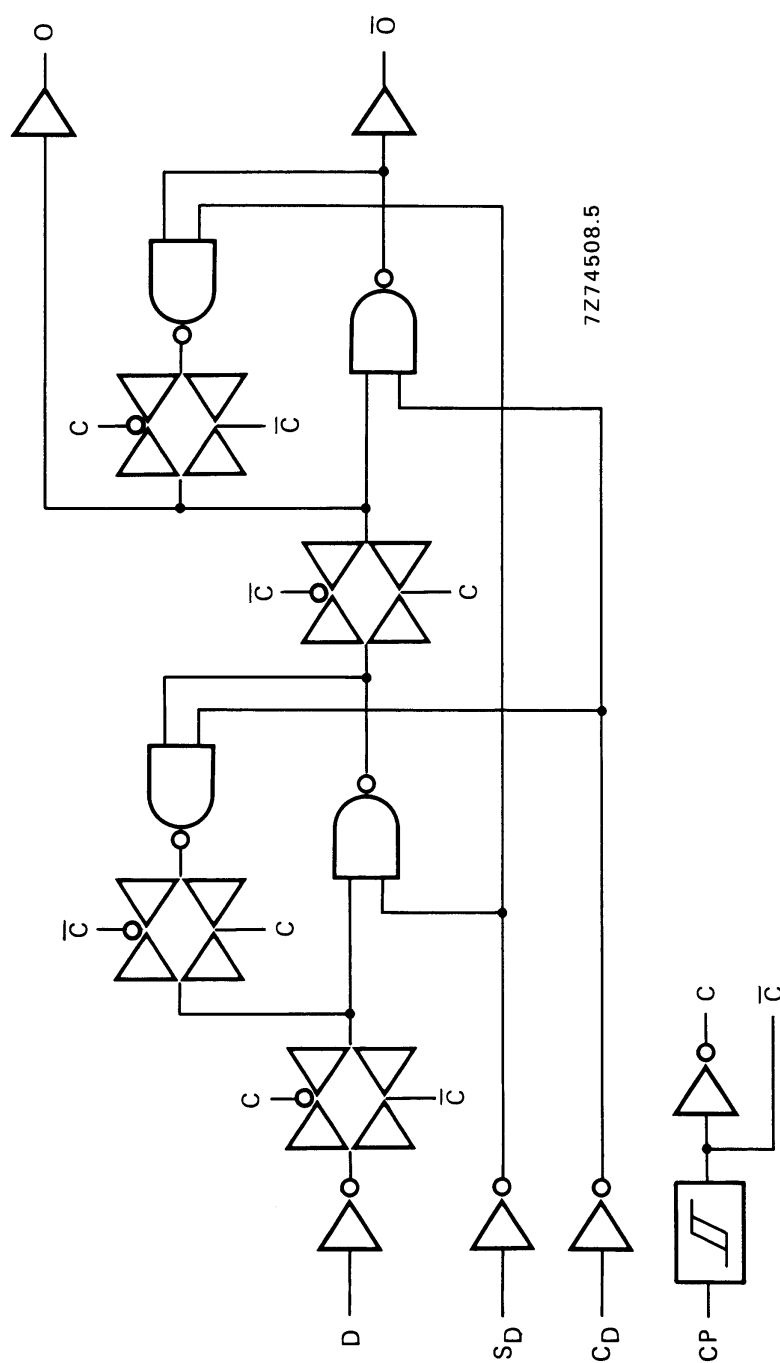


Fig.3 Logic diagram (one flip-flop).

Dual D-type flip-flop

HEF4013B
flip-flops

AC CHARACTERISTICS

 $V_{SS} = 0\text{ V}$; $T_{amb} = 25\text{ }^{\circ}\text{C}$; $C_L = 50\text{ pF}$; input transition times $\leq 20\text{ ns}$

	V _{DD} V	SYMBOL	MIN.	TYP.	MAX.	TYPICAL EXTRAPOLATION FORMULA	
Propagation delays CP → O, $\overline{O}$ HIGH to LOW	5 10 15	t _{PHL}		110 45 30	220 90 60 ns	83 ns + (0,55 ns/pF) C _L 34 ns + (0,23 ns/pF) C _L 22 ns + (0,16 ns/pF) C _L	
LOW to HIGH	5 10 15		t _{PLH}		95 40 30	190 80 60 ns	68 ns + (0,55 ns/pF) C _L 29 ns + (0,23 ns/pF) C _L 22 ns + (0,16 ns/pF) C _L
S _D → $\overline{O}$ HIGH to LOW	5 10 15			t _{PHL}		100 40 30	200 80 60 ns
S _D → O LOW to HIGH	5 10 15	t _{PLH}				75 35 25	150 70 50 ns
C _D → O HIGH to LOW	5 10 15		t _{PHL}			100 40 30	200 80 60 ns
C _D → $\overline{O}$ LOW to HIGH	5 10 15			t _{PLH}		60 30 20	120 60 40 ns
Output transition times HIGH to LOW	5 10 15	t _{THL}			60 30 20	120 60 40 ns	10 ns + (1,0 ns/pF) C _L 9 ns + (0,42 ns/pF) C _L 6 ns + (0,28 ns/pF) C _L
LOW to HIGH	5 10 15		t _{TLH}		60 30 20	120 60 40 ns	10 ns + (1,0 ns/pF) C _L 9 ns + (0,42 ns/pF) C _L 6 ns + (0,28 ns/pF) C _L

Dual D-type flip-flop

HEF4013B
flip-flops

AC CHARACTERISTICS



$V_{SS} = 0\text{ V}$; $T_{amb} = 25\text{ }^{\circ}\text{C}$; $C_L = 50\text{ pF}$; input transition times $\leq 20\text{ ns}$

	V_{DD} V	SYMBOL	MIN.	TYP.	MAX.	
Set-up time D $\rightarrow$ CP	5 10 15	t_{su}	40 25 15	20 10 5	ns ns ns	see also waveforms Figs 4 and 5
Hold time D $\rightarrow$ CP	5 10 15	t_{hold}	20 20 15	0 0 0	ns ns ns	
Minimum clock pulse width; LOW	5 10 15	t_{WCPL}	60 30 20	30 15 10	ns ns ns	
Minimum S_D pulse width; HIGH	5 10 15	t_{WSDH}	50 24 20	25 12 10	ns ns ns	
Minimum C_D pulse width; HIGH	5 10 15	t_{WCDH}	50 24 20	25 12 10	ns ns ns	
Recovery time for S_D	5 10 15	t_{RSD}	15 15 15	-5 0 0	ns ns ns	
Recovery time for C_D	5 10 15	t_{RCD}	40 25 25	25 10 10	ns ns ns	
Maximum clock pulse frequency	5 10 15	f_{max}	7 14 20	14 28 40	MHz MHz MHz	

	V_{DD} V	TYPICAL FORMULA FOR P (μW)	
Dynamic power dissipation per package (P)	5 10 15	$850 f_i + \sum (f_o C_L) \times V_{DD}^2$ $3\,600 f_i + \sum (f_o C_L) \times V_{DD}^2$ $9\,000 f_i + \sum (f_o C_L) \times V_{DD}^2$	where f_i = input freq. (MHz) f_o = output freq. (MHz) C_L = total load cap. (pF) $\sum (f_o C_L)$ = sum of outputs V_{DD} = supply voltage (V)

Dual D-type flip-flop

HEF4013B
flip-flops

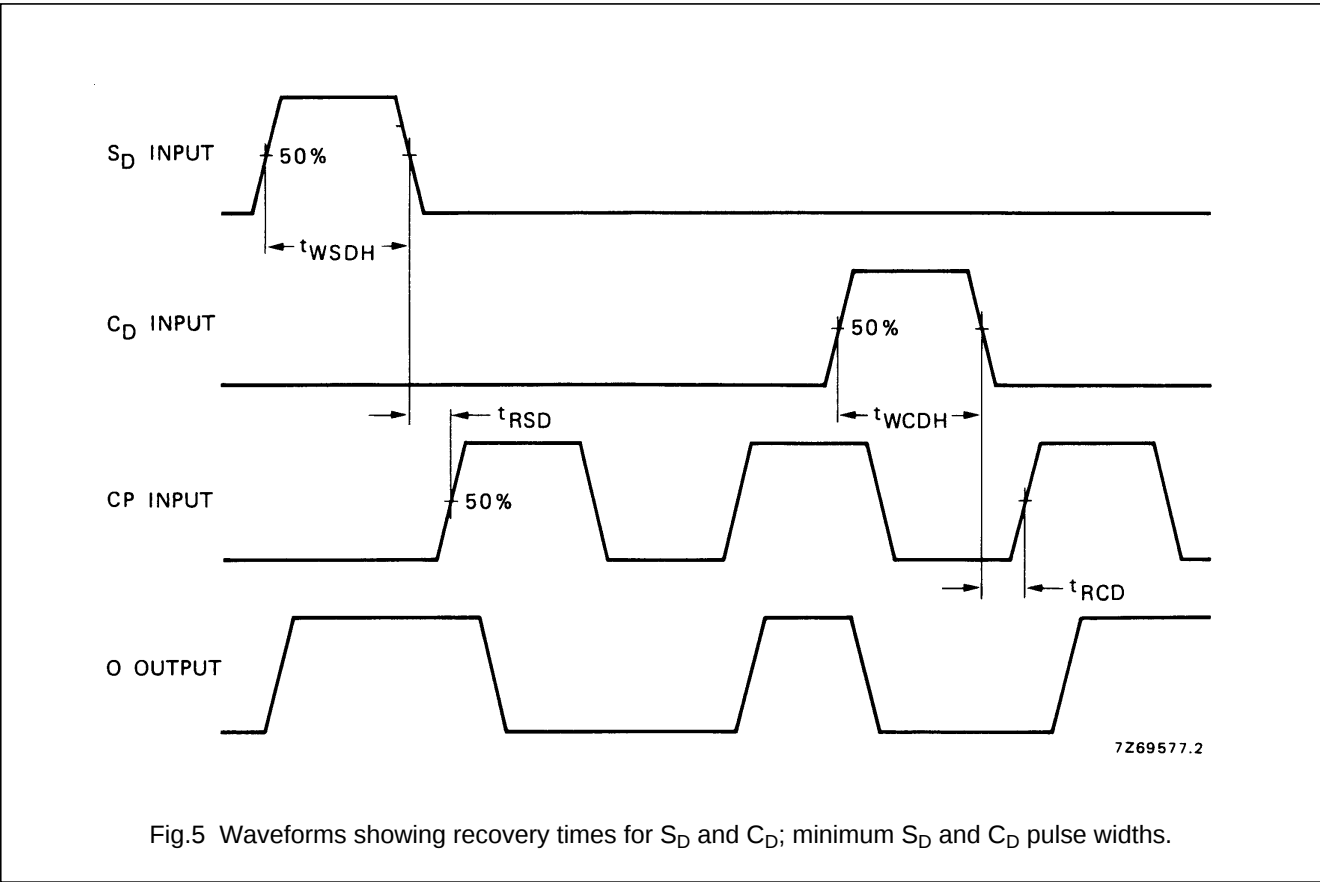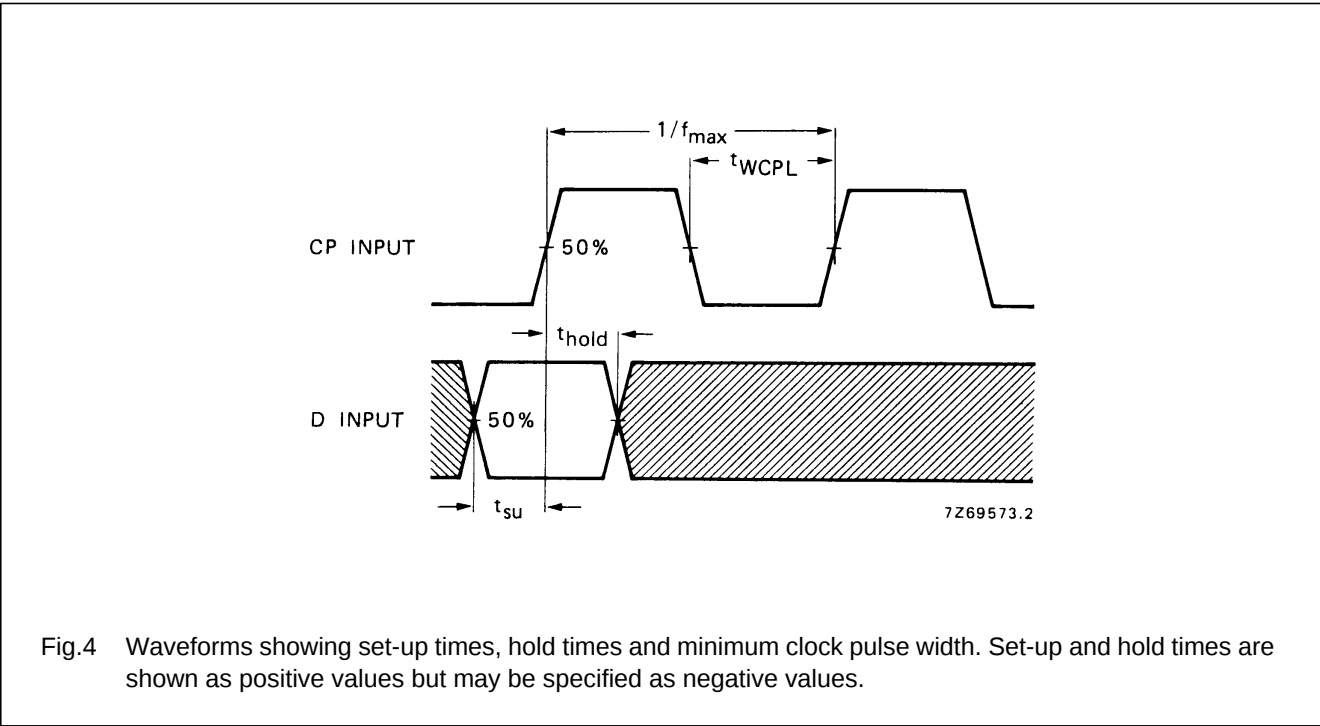

Dual D-type flip-flop

HEF4013B
flip-flops

APPLICATION INFORMATION

Some examples of applications for the HEF4013B are:

- Counters/dividers
- Registers
- Toggle flip-flops

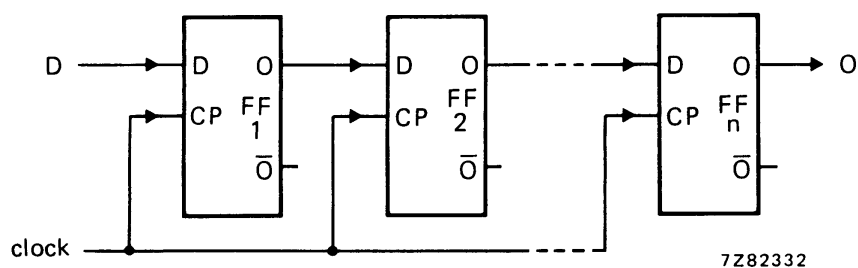


Fig.6 Typical application of the HEF4013B in an n-stage shift register.

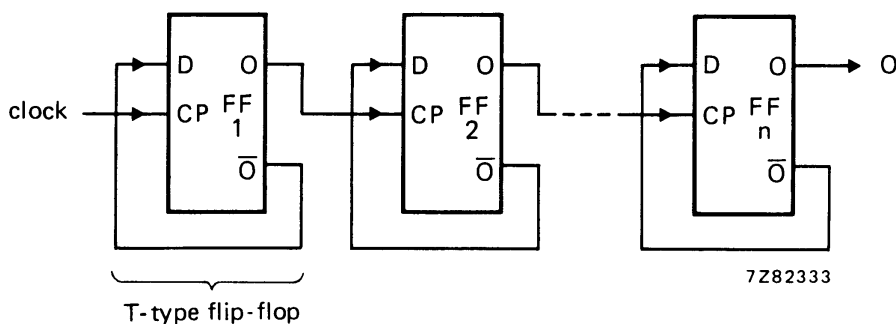


Fig.7 Typical application of the HEF4013B in a binary ripple up-counter; divide-by- 2^n .

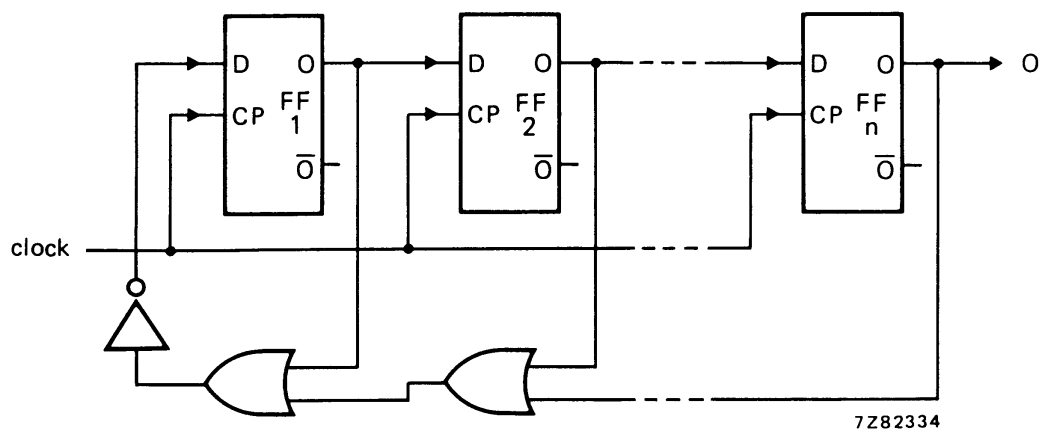


Fig.8 Typical application of the HEF4013B in a modified ring counter; divide-by-($n + 1$).

Copyright © Each Manufacturing Company.

All Datasheets cannot be modified without permission.

This datasheet has been download from :

www.AllDataSheet.com

100% Free DataSheet Search Site.

Free Download.

No Register.

Fast Search System.

www.AllDataSheet.com